

INTERNAL ASSESMENT- 2020
KANDI RAJ COLLEGE
DEPARTMENT OF PHYSICS

SEMESTER: 3rd
PAPER CODE: PHY-GCC-T-03

STREAM: Program Course (General)
Paper: Analog Systems and Applications

Full marks: 10

Answer Any Five questions of the following:

5×2=10

1. Draw the Energy Band Diagram of P-type and N-type Semiconductor.
2. What is Drift velocity of electrons?
3. Draw the circuit diagram of a full wave Bridge rectifier.
4. Why transistor is called current controlled device?
5. Draw the I-V characteristics of a PN- junction diode with proper circuit diagram.
6. Calculate the ripple factor of a half wave rectifier.
7. Define Q-point of a transistor. On what factors Q-point of a transistor depends?
8. Explain the Barkhausen criterion for sustained oscillation in case of an oscillator.

INTERNAL ASSESMENT 2020
KANDI RAJ COLLEGE
DEPARTMENT OF PHYSICS

SEMESTER: 3rd
PAPER CODE: PHY-G-SEC-T-01

STREAM: Program Course (General)
Paper: Electrical Circuits and Network Skill

Full marks: 5

Answer any five questions:

5×1=5

1. Which is more dangerous AC or DC?
2. What is a voltmeter? How it works?
3. What is single phase AC?
4. Write down the basic principle of DC motor.
5. What is a circuit breaker and how it works?
6. What are the Star and delta connection?
7. What are the advantages of AC generator over DC generator?

