

KANDI RAJ COLLEGE
2nd SEMSETER INTERNAL EXAMINATION 2021
PROGRAMME (COMPUTER SCIENCE)
COMPUTER SYSTEM ARCHITECTURE [UG-CC-L-201B/CC-1B]

TIME -45 minutes

ANSWER ANY TWO QUESTIONS:

(5X2=10)

1. Define Boolean Algebra ? Write down the rules for subtraction by 2's complement.
2. What is CMOS? Write short notes on RISC Architecture.
3. What is Flip-Flop? What is Truth Table? Explain half adder.
4. Write short notes on i) Encoder or ii) Decoder