

## U.G. 4th Semester Examination - 2021

**PHYSICS**

[HONOURS]

Course Code : PHY-H-CC-T-10

Full Marks : 20

Time : 1 Hour

*The figures in the right-hand margin indicate marks.  
Candidates are required to give their answers in their  
own words as far as practicable.*

**GROUP-A**

1. Answer any **five** questions: 1×5=5
  - a) Write down Barkhausen's criterion for self-sustained oscillations.
  - b) Explain how barrier potential is set up in a p-n junction diode.
  - c) Define CMRR for an OPAMP.
  - d) Define peak inverse voltage for a diode.
  - e) What do you understand by an ideal diode? Draw its VI characteristics.
  - f) Explain the term thermal runaway regarding BJT.
  - g) Draw the circuit diagram of a class-B Push-Pull amplifier using transistor.
  - h) Draw a circuit diagram of an emitter follower.

[Turn over]

**GROUP-B**

2. Answer any **one** question: 5×1=5
  - a) Define bandwidth of an amplifier. If  $f_l$  and  $f_h$  are the lower and upper half power frequencies of one amplifying stage find the corresponding values for N stages. 2+3
  - b) Draw self bias circuit for BJT. Explain how the bias curve is used to find the Q-point of the circuit. 1+4
  - c) Discuss the two-port representation of a transistor and hence define the h-parameters. 1+4

**GROUP-C**

3. Answer any **one** question: 10×1=10
  - a) Write down the properties of an ideal OP-AMP. What do you mean by virtual ground? Design a circuit using one or more OPAMP whose output is given by  $v_o = (2v_1 + 16v_2)$  where  $v_1$  and  $v_2$  are two inputs. Draw a simple circuit diagram of an integrator using OPAMP. 2+2+4+2

- b) Define loop gain for a feedback circuit. Describe Hartley oscillator with a circuit diagram. Hence find the expression for the frequency of oscillation. 2+3+5
- c) What do you mean by A/D conversion? Draw circuit diagram of a D/A converter using R-2R ladder and find out the expression of output. 2+3+5

-----